

EC452 Ultra High Frequency Techniques

Title: Prelab 2

Name: Shihyuan Yeh

UIN: 423008134

1. Quarter-Wave Transformer

Microstrip width of the 50Ω transmission = 4.92mm

Microstrip width of the 200Ω transmission = 0.17mm

For the $\lambda/4$ matching T-Line, $Z_{OT}=100\Omega$, so the width of the transmission line = 1.41mm and the length = 23.04mm

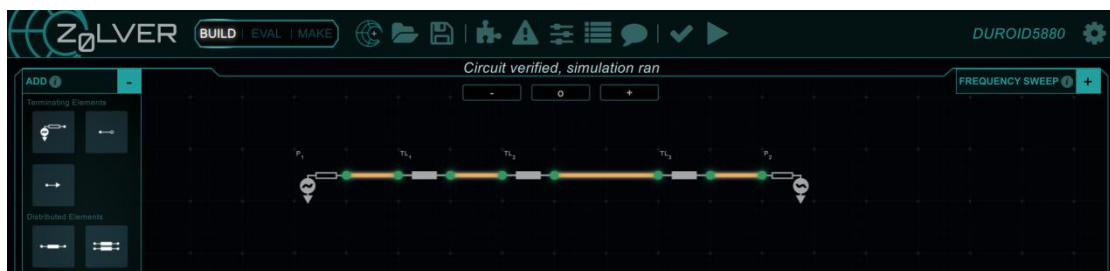


Figure 1 - A Quarter-Wave Transformer Design Layout in Z0lver

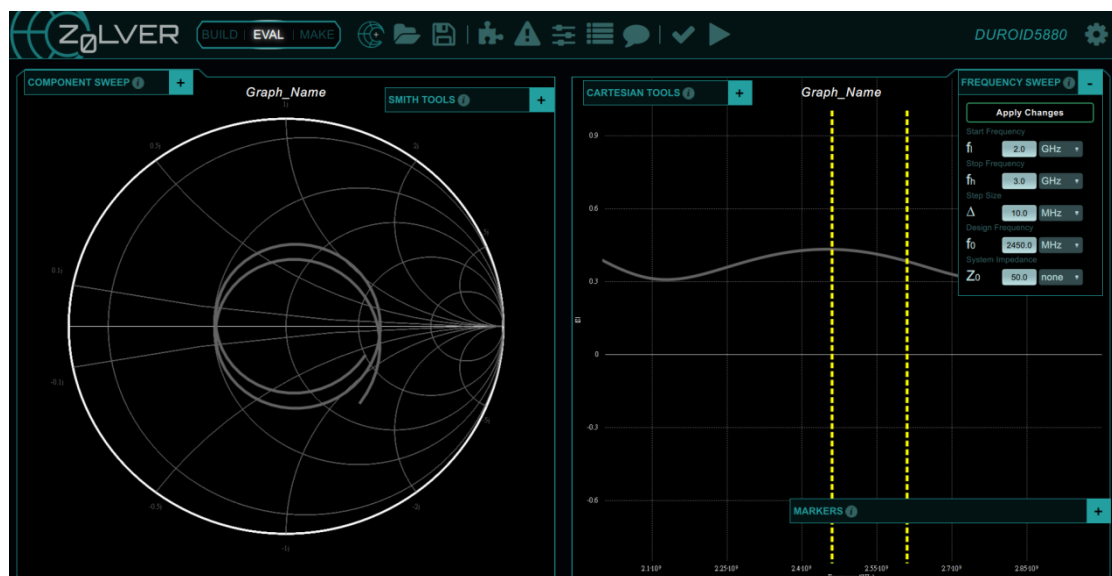


Figure 2 - S11 Simulation Results in Z0lver



Figure 3 - Circuit Layout on Duroid 5880 Substrate in Z0lver

2. Double-Stub matching network

$$Z_L=100-50j, z_L=2-j, y_L=0.4+0.2j$$

$$\text{Set } d_1=0.5\lambda, d_2=\lambda/8$$

$$y_1=0.4+0.2j, y_1'=0.4+1.8j$$

$$jb_1=0j, jb_1'=1.6j$$

$$\text{Rotate } d_2=0.125\lambda \Rightarrow jb_2=-1.05j, jb_2'=2.8j$$

$$1^{\text{st}} \text{ solution: } d_1=0.5\lambda, l_1=0\lambda, d_2=0.125\lambda, l_2=0.372\lambda$$

$$2^{\text{nd}} \text{ solution: } d_1'=0.5\lambda, l_1'=0.16\lambda, d_2'=0.125\lambda, l_2'=0.195\lambda$$

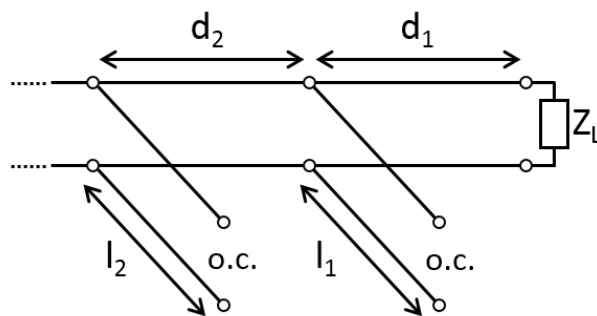


Figure 4 - A Double-Stub Matching Design Layout


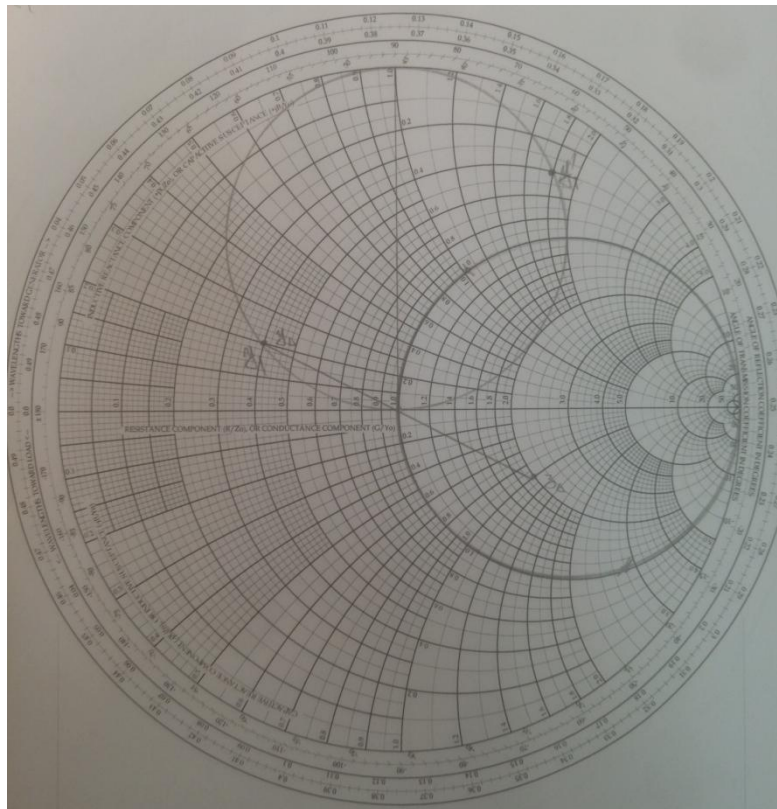
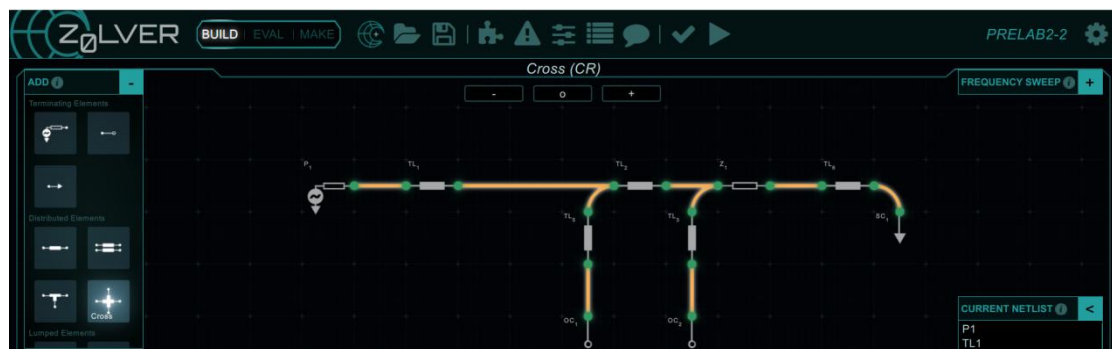


Figure 5 - Smith Chart Degian - 1

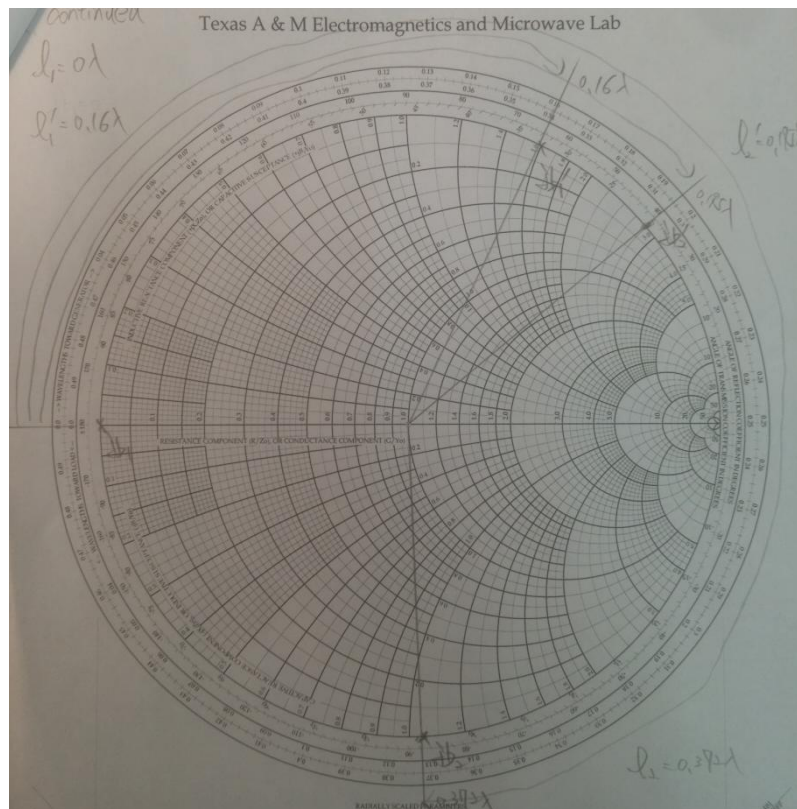

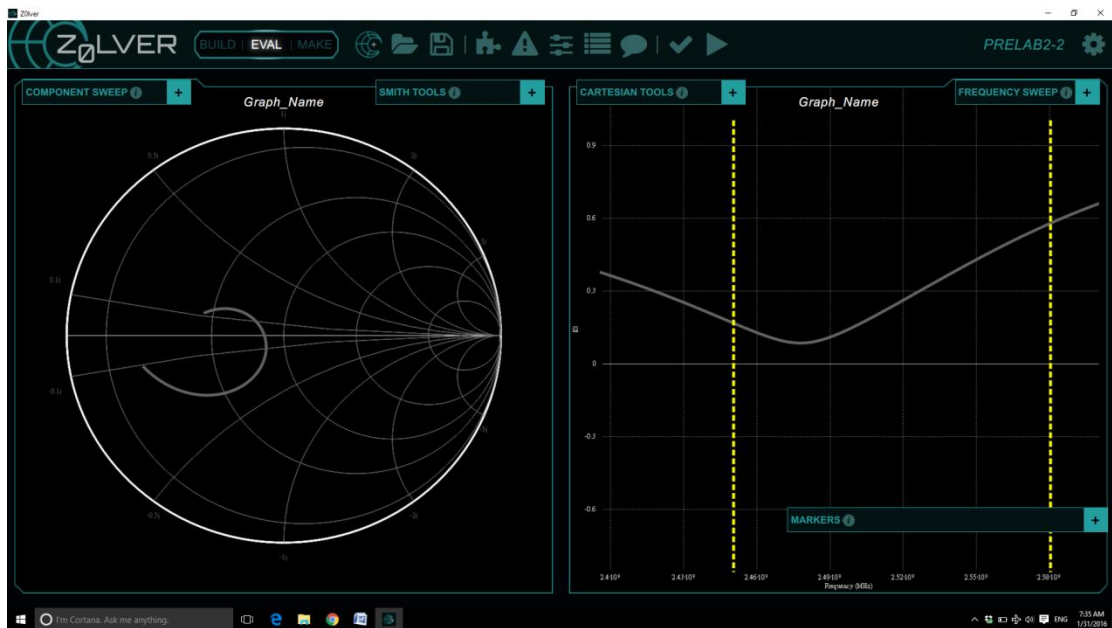


Figure 8 - S_{11} Simulation Results in Z0lver

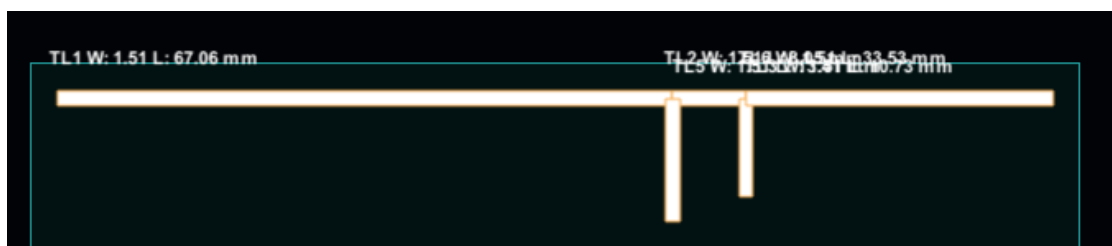


Figure 9 - Circuit Layout on FR4 Substrate in Z0lver