

# EC452 Ultra High Frequency Techniques

Title: Lab 1 - Laboratory Best Practices

Instructor: Dr. Gregory Huff

Student: Shihyuan Yeh

UIN: 423008134

Date: 02/10/2016

1.Demonstrate the operation of your Python installation by running the plotting program using the three datasets provided in “ECEN\_452\_Plotting.zip”

Ans:

```

jupyter Untitled2 Last Checkpoint: 5 minutes ago (unsaved changes)
File Edit View Insert Cell Kernel Help Python 3

In [*]: import matplotlib.pyplot as plt
import csv

#***Note: In order to use this code, all of the columns in the .csv file must have the same length. If your columns have
# different lengths, simply repeat the last value in each of the shorter columns until they are all the same size.

#Initialize arrays for x, y1, y2, y3
x = []
y1 = []
y2 = []
y3 = []

##Read .csv data file
#replace quoted text below with filepath to your .csv file
with open('ECEN_452_PlottingTestData.csv') as csvfile:
    reader = csv.DictReader(csvfile)
    for row in reader:
        #items in '' below need to exactly match the entry in the first row of the columns in the .csv file
        #edit/add additional lines as needed for each column of data
        x.append(float(row['x']))
        y1.append(float(row['y1']))
        y2.append(float(row['y2']))
        y3.append(float(row['y3']))

##Plotting
plt.figure(1) #initialize plot1
ax1 = plt.subplot(111) #create axes handle for plot1
ax1.plot(x, y1, 'b', label='y1 Data') #plot y1 vs. x, solid-blue, add label for legend
ax1.plot(x, y2, '-r', label='y2 Data') #plot y2 vs. x, solid-red, add label for legend
ax1.plot(x, y3, '--r', label='y3 Data') #plot y3 vs. x, dashed-red, add label for legend
ax1.legend(loc=4) #add legend at location #4 (bottom-right corner)
plt.grid(b=True, which='both', color='0.65', linestyle='-') #add solid grey gridlines
plt.title('Python Test Plot') #add plot title
plt.xlabel('x-axis [units]') #add x-axis title
plt.ylabel('y-axis [units]') #add y-axis title
plt.show() #required to display plots

```

Figure 1 - The Python Code Edited in Anaconda

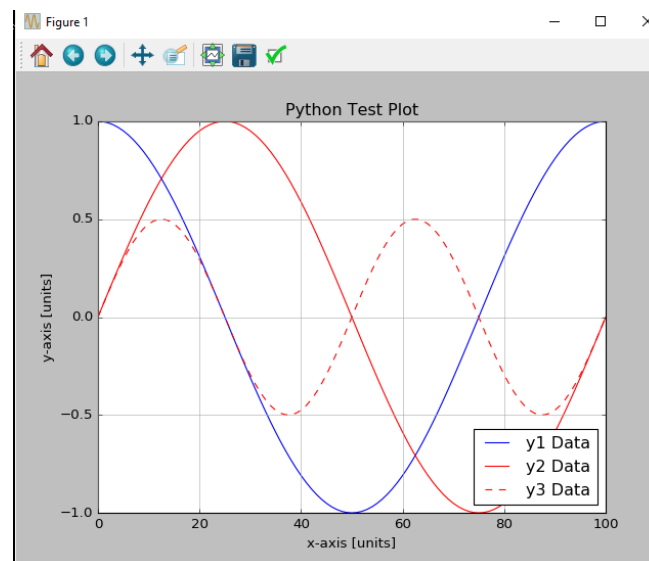


Figure 2 - The Plot of the Dataset

2.Email your GitHub account ID.

Ans: stevenyeh66

3.Familiarize yourself with the design and simulation environments in HFSS and Zolver by downloading and simulating the files “ECEN\_452\_Lab1.hfss”, “ECEN\_452\_Lab1a.zov”, and “ECEN\_452\_Lab1b.zov”.

Ans:

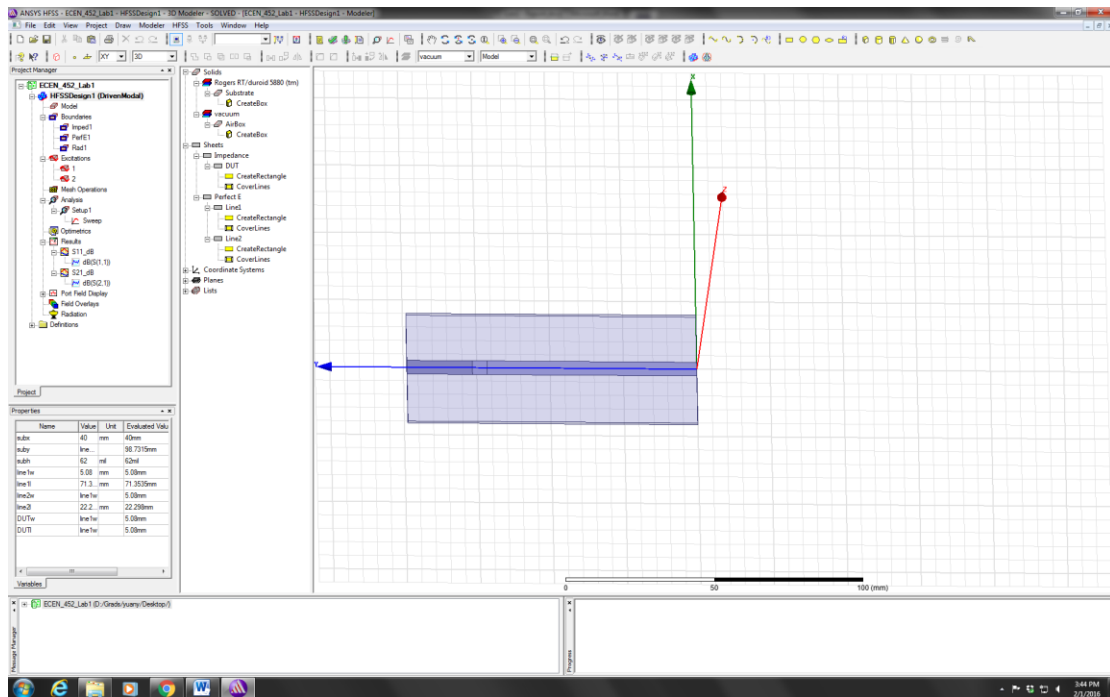


Figure 3 - The ECEN\_452\_Lab1.hfss Run in HFSS

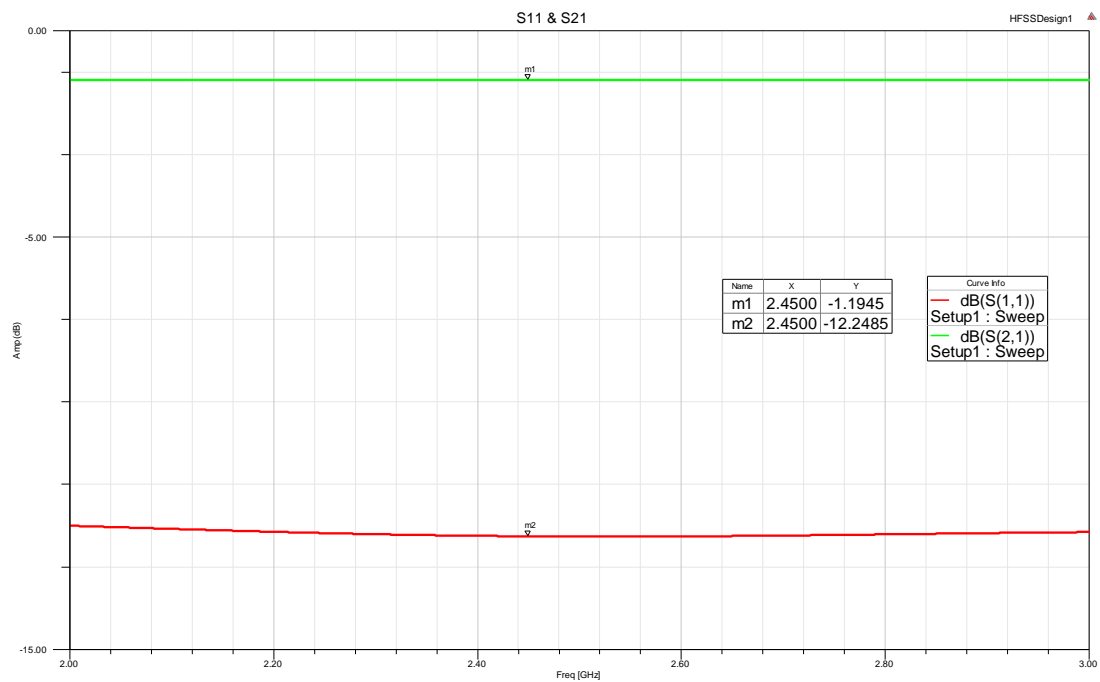


Figure 4 - The Simulation Results of the  $S_{11}$  and  $S_{21}$  Amplitude in dB

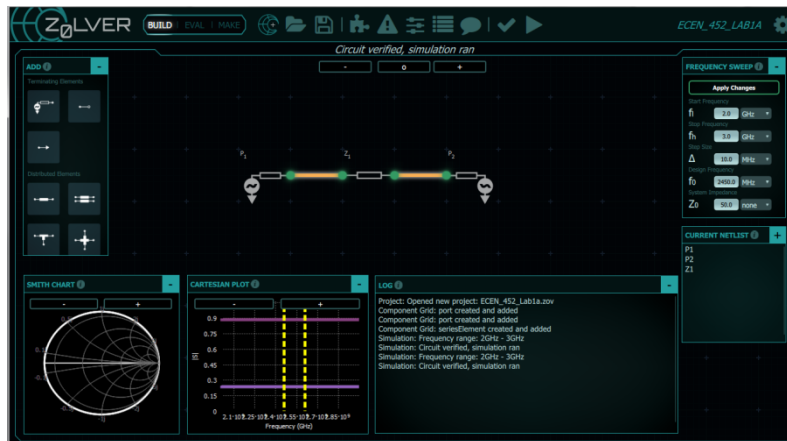


Figure 5 - The ECEN\_452\_Lab1a.zov Run in Z0lver

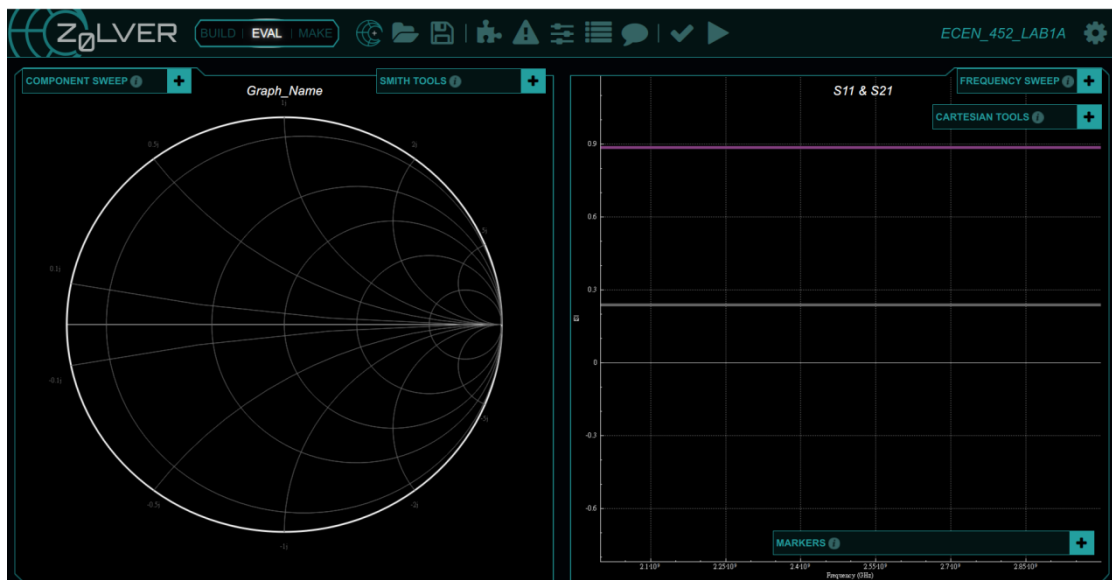


Figure 6 - The Simulation Results of S<sub>11</sub> and S<sub>21</sub> in Z0lver (ECEN\_452\_Lab1a.zov)

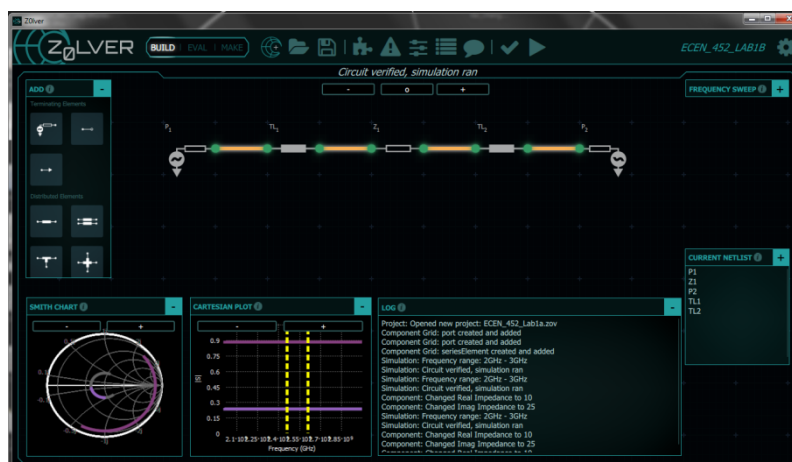


Figure 7 - The ECEN\_452\_Lab2a.zov Run in Z0lver

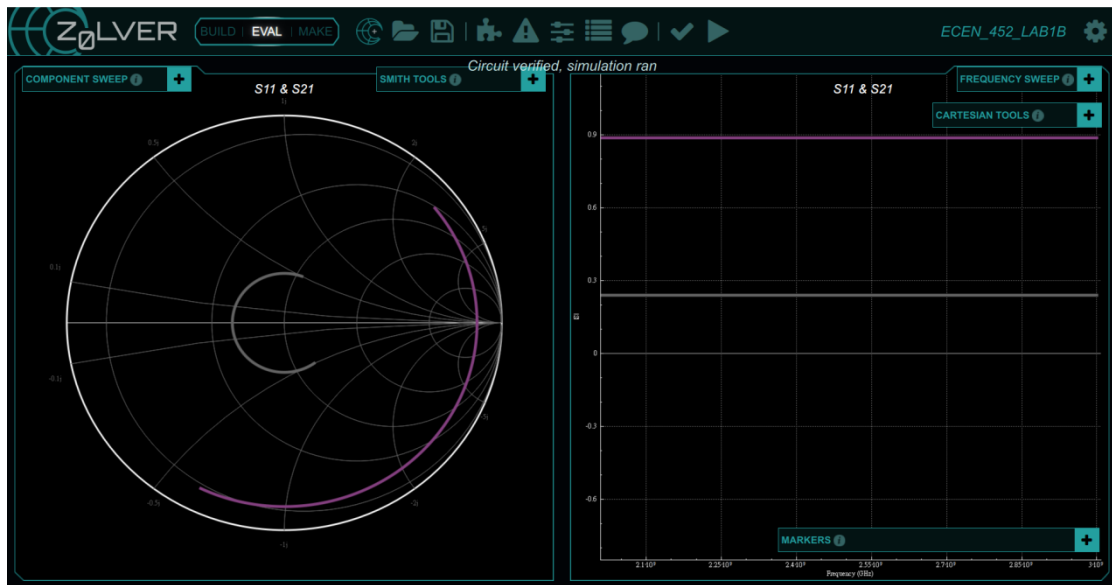


Figure 8 - The Simulation Results of  $S_{11}$  and  $S_{21}$  in Z0lver (ECEN\_452\_Lab2a.zov)

4. Calculate the two-port S and ABCD-matrices for a series impedance  $Z = 10 + 25j \, \Omega$  using a system impedance  $Z_0 = 50 \, \Omega$  and the frequency sweep parameters from the simulations.

Ans:

4.

$$\begin{array}{c} \text{---} Z_0 \text{---} \boxed{Z} \text{---} Z_0 \text{---} \\ | \quad \quad \quad | \\ \text{---} Z_0 \text{---} \quad \quad \quad \text{---} Z_0 \text{---} \end{array}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} 1 & 10 + 25j \\ 0 & 1 \end{bmatrix}$$

$$S = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} = \begin{bmatrix} \frac{A + B Y_0 - C Z_0 - D}{\Delta} & \frac{2(AD - BC)}{\Delta} \\ \frac{2}{\Delta} & \frac{-A + B Y_0 - C Z_0 + D}{\Delta} \end{bmatrix} = \begin{bmatrix} 0.24 \angle 35.39^\circ & 0.89 \angle -1.91^\circ \\ 0.89 \angle -1.91^\circ & 0.24 \angle 35.39^\circ \end{bmatrix}$$

$$Y_0 = \frac{1}{Z_0} = 0.02, \quad \Delta = A + B Y_0 + C Z_0 + D = 2.2 + 9.75j$$

5. Shift the reference planes of both matrices calculated in the previous problem by assuming they are connected to lossless lines of characteristic impedance  $Z_0 = 50 \, \Omega$  with a length  $0.8 \lambda$  at Port 1 and  $0.25 \lambda$  at Port 2.

Ans:

5. shift  $0.8\lambda$  @ port 1 & shift  $0.25\lambda$  @ port 2

$$\theta_1 = \beta_1 l_1 = \frac{2\pi}{\lambda} \times 0.8\lambda = 1.6\pi = 288^\circ$$

$$\theta_2 = \beta_2 l_2 = \frac{2\pi}{\lambda} \times 0.25\lambda = 90^\circ$$

$$[S'] = \begin{bmatrix} e^{-j\theta_1} & 0 \\ 0 & e^{-j\theta_2} \end{bmatrix} \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} e^{-j\theta_1} & 0 \\ 0 & e^{-j\theta_2} \end{bmatrix} = \begin{bmatrix} e^{-j\theta_1} S_{11} & e^{-j\theta_1} S_{12} \\ e^{-j\theta_2} S_{21} & e^{-j\theta_2} S_{22} \end{bmatrix} \begin{bmatrix} e^{-j\theta_1} & 0 \\ 0 & e^{-j\theta_2} \end{bmatrix}$$

$$= \begin{bmatrix} e^{-j\theta_1} S_{11} & e^{-j(\theta_1+\theta_2)} S_{12} \\ e^{-j(\theta_1+\theta_2)} S_{21} & e^{-j\theta_2} S_{22} \end{bmatrix} = \begin{bmatrix} e^{-j216^\circ} 0.24 & e^{-j338.9^\circ} \\ e^{-j18^\circ} 0.89 & e^{-j12.1^\circ} \\ e^{-j18^\circ} 0.89 & e^{-j12.1^\circ} \\ e^{-j216^\circ} 0.24 & e^{-j338.9^\circ} \end{bmatrix}$$

$$= \begin{bmatrix} e^{-j160.61^\circ} 0.24 & e^{-j130.1^\circ} 0.89 \\ e^{-j30.1^\circ} 0.89 & e^{-j144.61^\circ} 0.24 \end{bmatrix}$$

6. Create two separate plots comparing analytical, Z0lver, and HFSS; one with the magnitude of  $S_{11}$  in dB and the other with the magnitude of  $S_{21}$  in dB.

Ans:

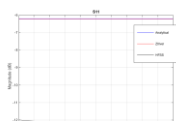


Figure 9 - Comparisons of  $S_{11}$  Between Analytical, Z0lver and HFSS

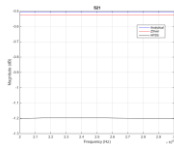


Figure 10 - Comparisons of  $S_{21}$  Between Analytical, Zolver and HFSS

7. Become familiar with the following substrates by filling out the table below.

	FR4	Duroid 5880	Duroid 6006	Duroid 6010.2
$\epsilon_r$	4.4	2.2	6.15	10.2
$\tan\delta$	0.02	9e-4	0.0027	0.0023

8. Fill in the table below by indicating which connector types can be mated (Y/N).

	Type N	SMA	3.5 mm	2.92 mm	2.4 mm	1.85 mm
Type N	Y	N	N	N	N	N
SMA	N	Y	Y	Y	N	N
3.5 mm	N	Y	Y	Y	N	N
2.92 mm	N	Y	Y	Y	N	N
2.4 mm	N	N	N	N	Y	Y
1.85 mm	N	N	N	N	Y	Y